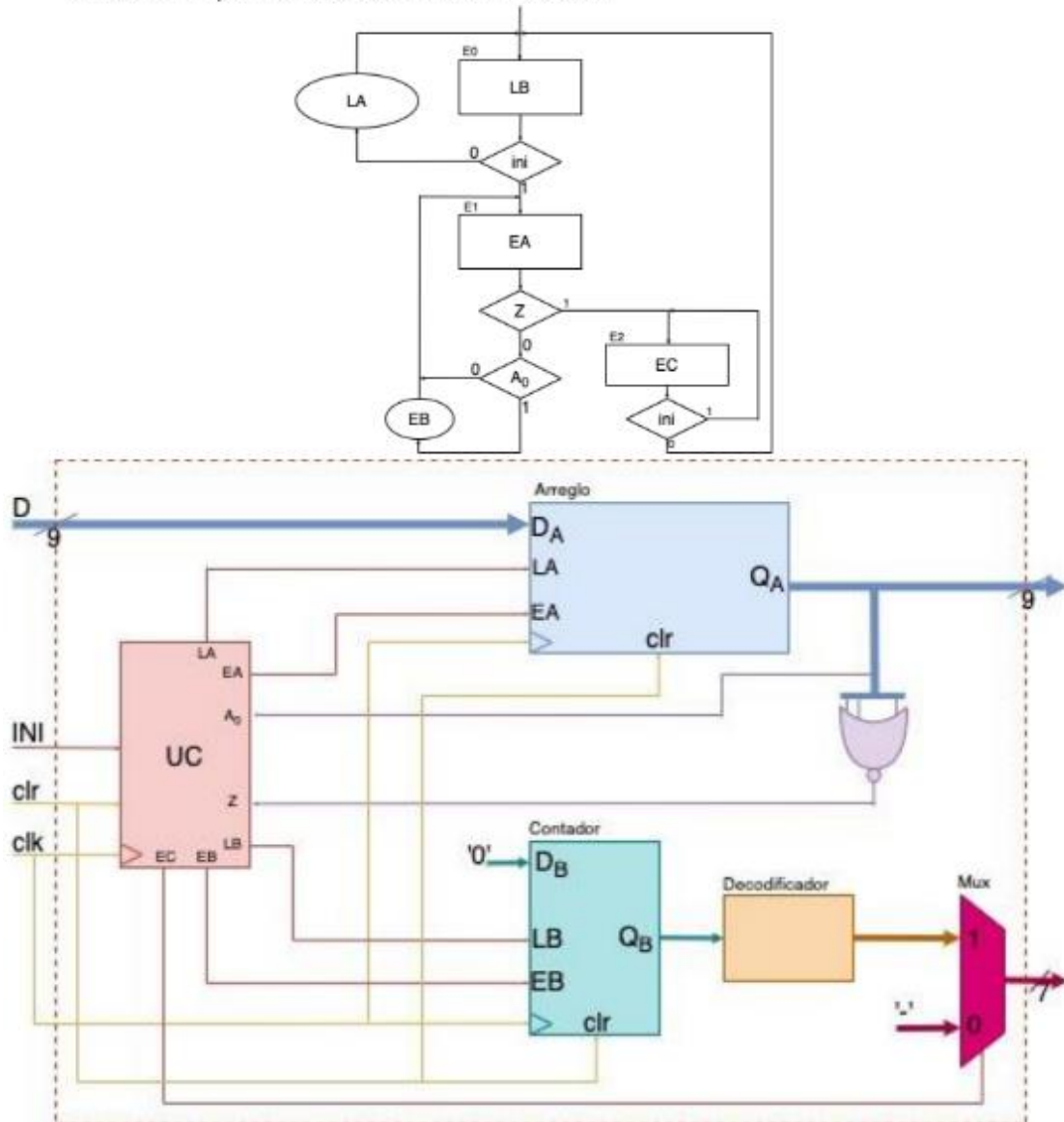


## Práctica 12

## Cartas ASM

1. Implemente la etapa arquitectura para encontrar el número de 1's en un arreglo de 9 localidades y mostrar el resultado en un display de 7 segmentos, de acuerdo con la siguiente arquitectura y lógica de control, tome en cuenta que la arquitectura debe ser implementada de manera modular.



2. Simular el funcionamiento de cada uno de los elementos mediante el uso de test-bench, utilice los estímulos necesarios para demostrar el correcto funcionamiento de cada elemento.

## Unidad de Control

## Código de implementación

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity ctrlUnit is
    Port(
        clr, clk: in std_logic;
        ini, z, a0: in std_logic;
        la, lb, ea, eb, ec : out std_logic);
end ctrlUnit;

architecture Behavioral of ctrlUnit is
    type estados is(E0, E1, E2);
    signal edo_act, edo_sig: estados;
begin
    process(clk, clr)
    begin
        if(clr = '1') then
            edo_act <= E0;
        elsif(rising_edge(clk)) then
            edo_act <= edo_sig;
        end if;
    end process;

    process(edo_act, ini, z, a0)
    begin
        la <= '0';
        lb <= '0';
        ea <= '0';
        eb <= '0';
        ec <= '0';
        case edo_act is

            when E0 =>
                lb <= '1';
                if(ini = '0') then
                    la <= '1';
                    edo_sig <= E0;
                else
                    edo_sig <= E1;
                end if;

            when E1 =>
                ea <= '1';
                if (z = '0') then
                    if (a0 = '0') then
                        edo_sig <= E1;
```

```

        else
            eb <= '1';
            edo_sig <= E1;
        end if;
    else
        edo_sig <= E2;
    end if;

    when E2 =>
        ec <= '1';
        if (ini = '0') then
            edo_sig <= E0;
        else
            edo_sig <= E2;
        end if;
    end case;
end process;
end Behavioral;

```

Código de simulación y forma de onda

```

library ieee;
use ieee.std_logic_1164.all;

entity tb_ctrlUnit is
end tb_ctrlUnit;

architecture tb of tb_ctrlUnit is

    component ctrlUnit
        port (clr : in std_logic;
              clk : in std_logic;
              ini : in std_logic;
              z   : in std_logic;
              a0  : in std_logic;
              la   : out std_logic;
              lb   : out std_logic;
              ea   : out std_logic;
              eb   : out std_logic;
              ec   : out std_logic);
    end component;

    signal clr : std_logic;
    signal clk : std_logic;
    signal ini : std_logic;
    signal z   : std_logic;
    signal a0  : std_logic;
    signal la  : std_logic;
    signal lb  : std_logic;

```

```
signal ea : std_logic;
signal eb : std_logic;
signal ec : std_logic;

constant TbPeriod : time := 1000 ns; -- EDIT Put right period here
signal TbClock : std_logic := '0';
signal TbSimEnded : std_logic := '0';

begin

    dut : ctrlUnit
    port map (clr => clr,
              clk => clk,
              ini => ini,
              z  => z,
              a0 => a0,
              la => la,
              lb => lb,
              ea => ea,
              eb => eb,
              ec => ec);

    -- Clock generation
    TbClock <= not TbClock after TbPeriod/2 when TbSimEnded /= '1' else '0';

    -- EDIT: Check that clk is really your main clock signal
    clk <= TbClock;

    stimuli : process
    begin
        -- EDIT Adapt initialization as needed
        clr <= '0';
        ini <= '1';
        z <= '0';
        a0 <= '1';

        -- EDIT Add stimuli here
        wait for 100 * TbPeriod;

        -- Stop the clock and hence terminate the simulation
        TbSimEnded <= '1';
        wait;
    end process;

end tb;
```


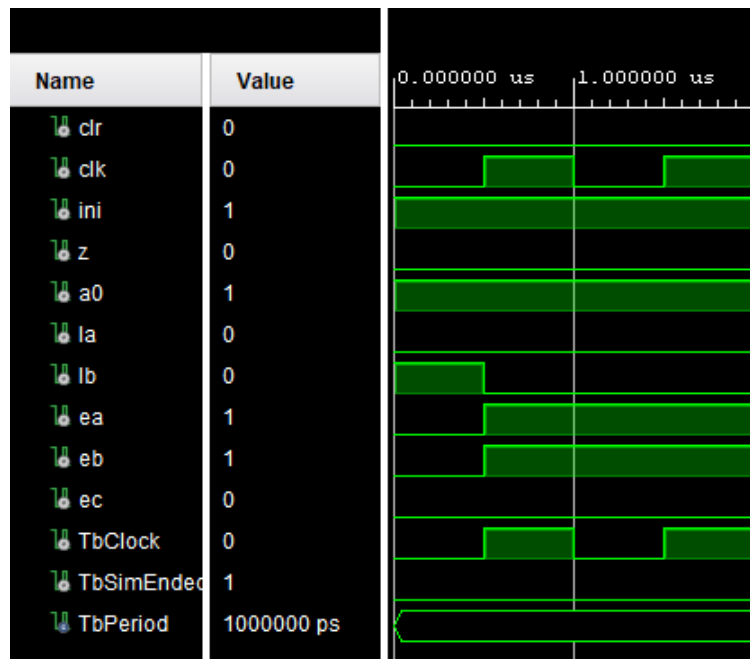


Diagrama RTL

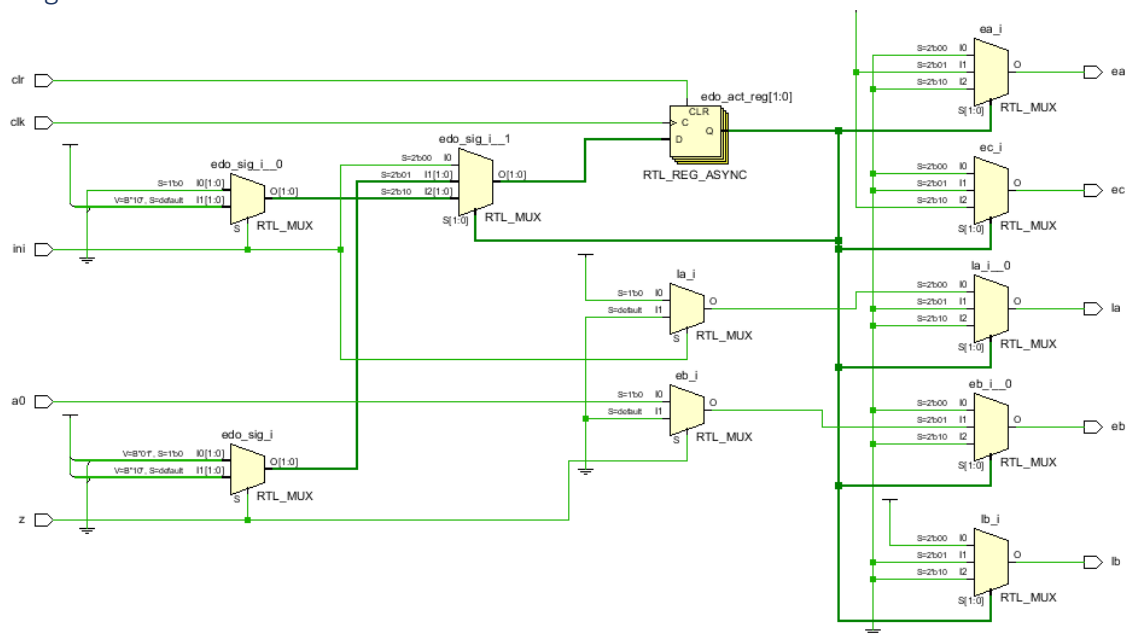

## Registro

## Código de implementación

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity arreglo is
Port ( la, ea, clk, clr : in  STD_LOGIC;
      dato : in  STD_LOGIC_VECTOR (8 downto 0);
      dato1 : out  STD_LOGIC_VECTOR (8 downto 0);
      z, a0 : out  STD_LOGIC);

```

```

end arreglo;

architecture Behavioral of arreglo is

signal a: STD_LOGIC_VECTOR (8 downto 0);
begin
    process (clk, clr)
    begin
        if (clr = '1') then
            a<="000000000";
        elsif (clk'event and clk = '1') then
            if (la = '1' and ea = '0') then
                a <= dato;
            end if;
            if (la = '0' and ea = '1') then
                a <= to_stdlogicvector(to_bitvector(a) srl 1);
            end if;
        end if;
    end process;
    dato1 <= a;
    a0 <= a(0);
    z <= not(a(0) or a(1) or a(2) or a(3) or a(4) or a(5) or a(6) or a(7)
or a(8));

end Behavioral;

```

Código de simulación y forma de onda

```

library ieee;
use ieee.std_logic_1164.all;

entity tb_arreglo is
end tb_arreglo;

architecture tb of tb_arreglo is

    component arreglo
        port (la      : in std_logic;
              ea      : in std_logic;
              clk     : in std_logic;
              clr     : in std_logic;
              dato     : in std_logic_vector (8 downto 0);
              salida   : out std_logic_vector (8 downto 0);
              z        : out std_logic;
              a0       : out std_logic);
    end component;

    signal la      : std_logic;

```

```
signal ea    : std_logic;
signal clk   : std_logic;
signal clr   : std_logic;
signal dato  : std_logic_vector (8 downto 0);
signal salida : std_logic_vector (8 downto 0);
signal z     : std_logic;
signal a0    : std_logic;

constant TbPeriod : time := 10 ns; -- EDIT Put right period here
signal TbClock : std_logic := '0';
signal TbSimEnded : std_logic := '0';

begin

    dut : arreglo
    port map (la    => la,
              ea    => ea,
              clk   => clk,
              clr   => clr,
              dato  => dato,
              salida => salida,
              z     => z,
              a0    => a0);

    TbClock <= not TbClock after TbPeriod/2 when TbSimEnded /= '1' else '0';

    -- EDIT: Check that clk is really your main clock signal
    clk <= TbClock;

    stimuli : process
    begin

        wait for 10 ns;
        dato<= "111111111";
        la <= '1';
        ea <= '0';
        clr<= '0';
        wait for 10 ns;
        clr <= '0';
        la<= '0';
        ea <= '1';
        wait for 10ns;
        la <= '0';
        ea <= '1';
        wait for 10ns;
        la <= '0';
        ea <= '1';
        wait for 10ns;
        la <= '0';
```

```

        ea <= '1';
        wait for 10ns;
        wait;
    end process;

end tb;

```


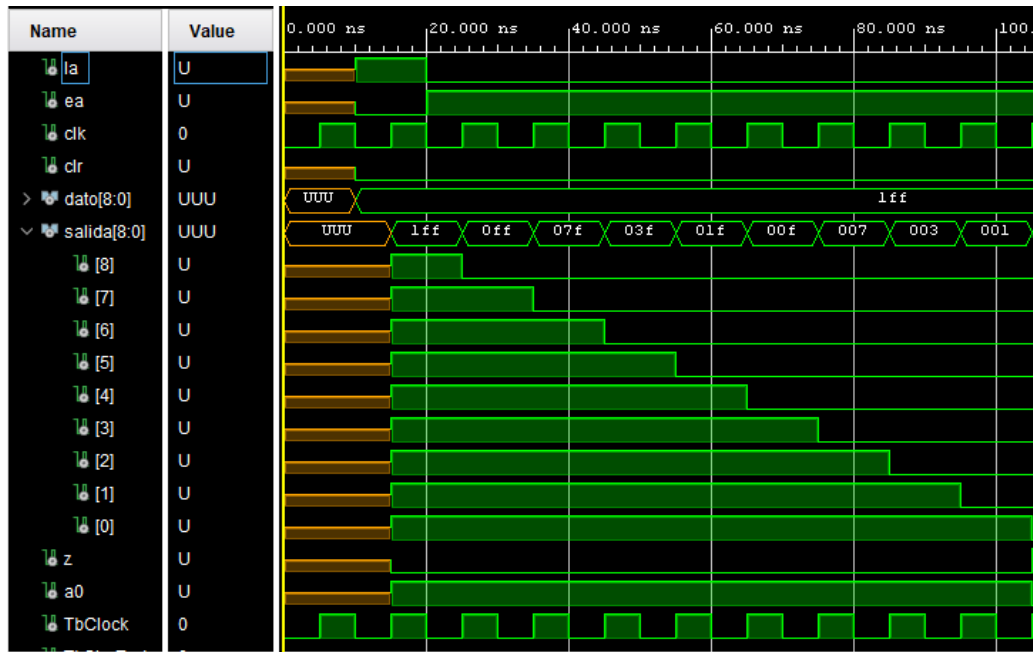


Diagrama RTL

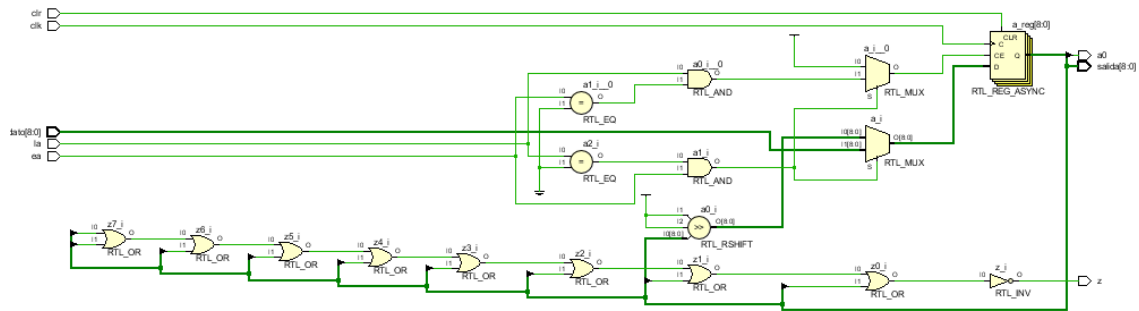

## Contador

### Código de implementación

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity Contador is
Port ( clk, clr : in  STD_LOGIC;

```



```

    lb, eb : in  STD_LOGIC;
    B : inout  STD_LOGIC_VECTOR (3 downto 0));
end Contador;

architecture Behavioral of Contador is

begin

    process(clk,clr)
    begin
        if(clr = '1' ) then
            B <= "0000";
        elsif(clk'event and clk = '1' ) then
            if(eb = '0' and lb = '1') then
                B <= "0000";
            elsif(eb = '1' and lb = '0' ) then
                B <= B + 1;
            end if;
        end if;
    end process;

end Behavioral;

```

Código de simulación y forma de onda

```

library ieee;
use ieee.std_logic_1164.all;

entity tb_Contador is
end tb_Contador;

architecture tb of tb_Contador is

    component Contador
        port (clk : in std_logic;
              clr : in std_logic;
              lb  : in std_logic;
              eb  : in std_logic;
              B   : inout std_logic_vector (3 downto 0));
    end component;

    signal clk : std_logic;
    signal clr : std_logic;
    signal lb  : std_logic;
    signal eb  : std_logic;
    signal B   : std_logic_vector (3 downto 0);

```

```
constant TbPeriod : time := 100 ns; -- EDIT Put right period here
signal TbClock : std_logic := '0';
signal TbSimEnded : std_logic := '0';

begin
    dut : Contador
    port map (clk => clk,
              clr => clr,
              lb  => lb,
              eb  => eb,
              B   => B);
    -- Clock generation
    TbClock <= not TbClock after TbPeriod/2 when TbSimEnded /= '1' else '0';

    -- EDIT: Check that clk is really your main clock signal
    clk <= TbClock;

    stimuli : process
    begin
        -- EDIT Adapt initialization as needed
        wait for 10ns;
        clr <= '0';
        wait for 100ns;
        lb <= '1';
        eb <= '0';
        wait for 100ns;
        lb <= '0';
        eb <= '1';
        wait for 100ns;
        lb <= '0';
        eb <= '0';
        wait for 100ns;
        lb <= '0';
        eb <= '1';
        wait for 200ns;
        lb <= '0';
        eb <= '0';
        wait for 100ns;
        -- EDIT Add stimuli here
        wait for 100 * TbPeriod;
        -- Stop the clock and hence terminate the simulation
        TbSimEnded <= '1';
        wait;
    end process;
end tb;
```


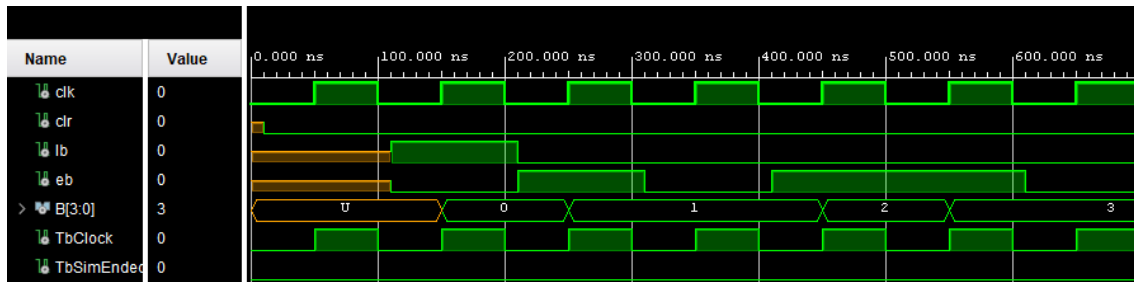


Diagrama RTL

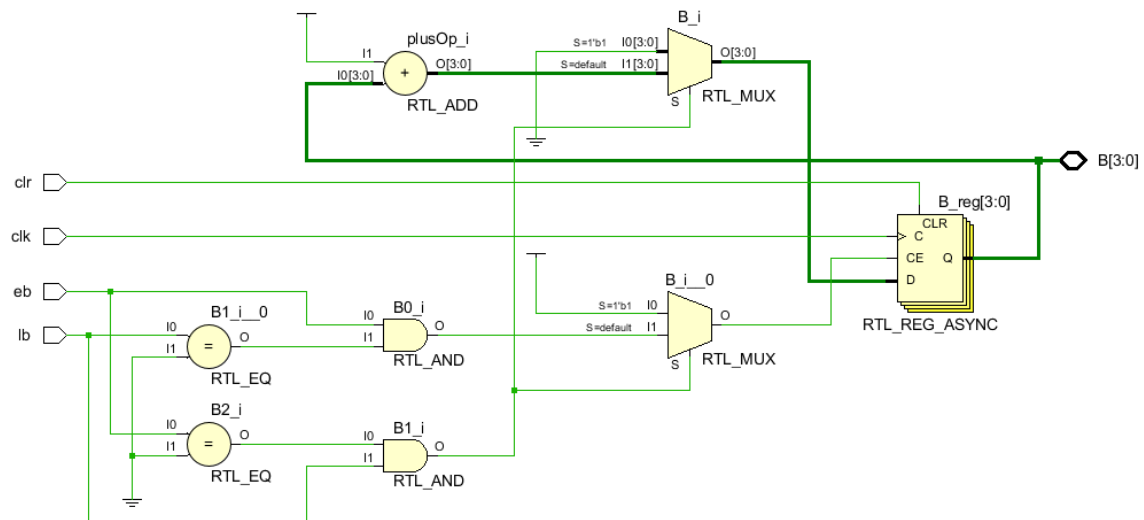

## Multiplexor

Código de implementación

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity multiplexor is
  Port ( aux : in  STD_LOGIC_VECTOR (6 downto 0);
        ec : in  STD_LOGIC;
        display : out  STD_LOGIC_VECTOR (6 downto 0));
end multiplexor;

architecture Behavioral of multiplexor is

  constant guion : std_logic_vector(6 downto 0) := "1111110";

begin

  with ec select
    display <= guion when '0',
              aux when others;

end Behavioral;

```

Código de simulación y forma de onda

```
library ieee;
use ieee.std_logic_1164.all;

entity tb_multiplexor is
end tb_multiplexor;

architecture tb of tb_multiplexor is

    component multiplexor
        port (aux      : in std_logic_vector (6 downto 0);
              ec       : in std_logic;
              display   : out std_logic_vector (6 downto 0));
    end component;

    signal aux      : std_logic_vector (6 downto 0);
    signal ec       : std_logic;
    signal display  : std_logic_vector (6 downto 0);

    constant TbPeriod : time := 10 ns; -- EDIT Put right period here
    signal TbClock    : std_logic := '0';
    signal TbSimEnded : std_logic := '0';

begin

    dut : multiplexor
    port map (aux      => aux,
              ec       => ec,
              display => display);

    -- Clock generation
    TbClock <= not TbClock after TbPeriod/2 when TbSimEnded /= '1' else '0';

    stimuli : process
    begin
        wait for 10ns;
        aux <= "1001111";
        ec <= '0';
        wait for 10ns;
        ec <= '1';
        wait for 10ns;

        -- EDIT Add stimuli here
        wait for 100 * TbPeriod;
        -- Stop the clock and hence terminate the simulation
        TbSimEnded <= '1';
        wait;
    end process;

end tb;
```


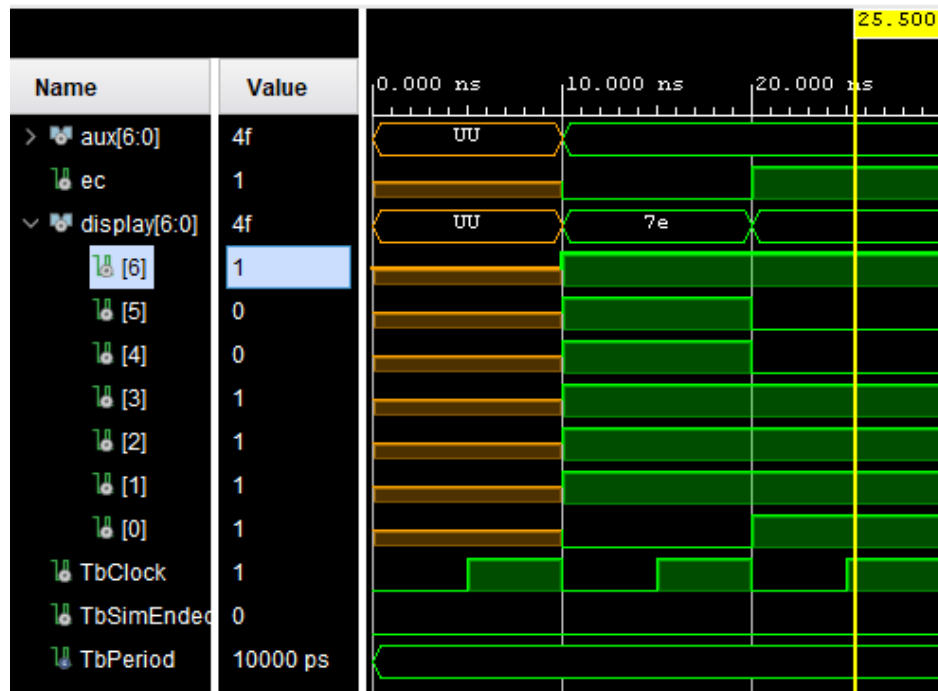


Diagrama RTL

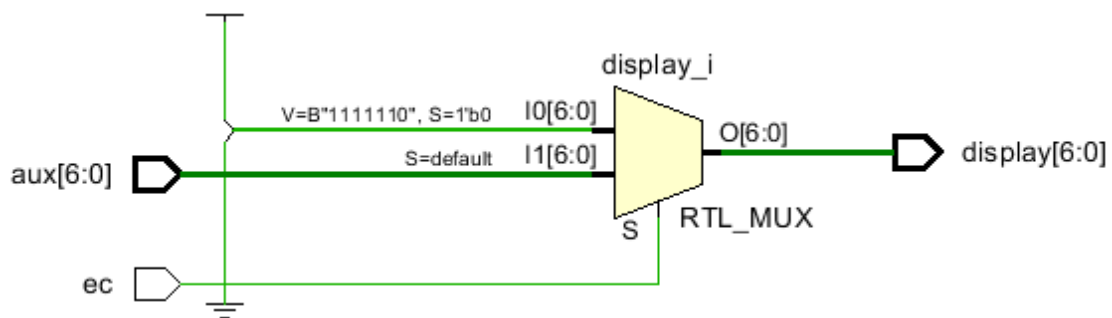

## Decodificador

Código de implementación

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Decodificador is
Port ( B : in  STD_LOGIC_VECTOR (3 downto 0);
      aux : out STD_LOGIC_VECTOR (6 downto 0));
end Decodificador;

architecture Behavioral of Decodificador is

    constant num_0 : std_logic_vector(6 downto 0) := "0000001";
    constant num_1 : std_logic_vector(6 downto 0) := "1001111";
    constant num_2 : std_logic_vector(6 downto 0) := "0010010";


```

```

constant num_3 : std_logic_vector(6 downto 0) := "0000110";
constant num_4 : std_logic_vector(6 downto 0) := "1001100";
constant num_5 : std_logic_vector(6 downto 0) := "0100100";
constant num_6 : std_logic_vector(6 downto 0) := "0100000";
constant num_7 : std_logic_vector(6 downto 0) := "0001111";
constant num_8 : std_logic_vector(6 downto 0) := "0000000";
constant num_9 : std_logic_vector(6 downto 0) := "0000100";
constant guion : std_logic_vector(6 downto 0) := "1111110";
begin

    with B select
        aux <= num_0 when "0000",
              num_1 when "0001",
              num_2 when "0010",
              num_3 when "0011",
              num_4 when "0100",
              num_5 when "0101",
              num_6 when "0110",
              num_7 when "0111",
              num_8 when "1000",
              num_9 when "1001",
              guion when others;
end Behavioral;

```

Código de simulación y forma de onda

```

library ieee;
use ieee.std_logic_1164.all;

entity tb_Decodificador is
end tb_Decodificador;

architecture tb of tb_Decodificador is

    component Decodificador
        port (B : in std_logic_vector (3 downto 0);
              aux : out std_logic_vector (6 downto 0));
    end component;

    signal B : std_logic_vector (3 downto 0);
    signal aux : std_logic_vector (6 downto 0);

    constant TbPeriod : time := 10 ns; -- EDIT Put right period here
    signal TbClock : std_logic := '0';
    signal TbSimEnded : std_logic := '0';

begin

    dut : Decodificador

```

```

port map (B    => B,
          aux  => aux);
-- Clock generation
TbClock <= not TbClock after TbPeriod/2 when TbSimEnded /= '1' else '0';

stimuli : process
begin
    -- EDIT Adapt initialization as needed
    wait for 10ns;
    B <= "0010";
    wait for 10ns;

    -- EDIT Add stimuli here
    wait for 100 * TbPeriod;

    -- Stop the clock and hence terminate the simulation
    TbSimEnded <= '1';
    wait;
end process;

end tb;

```


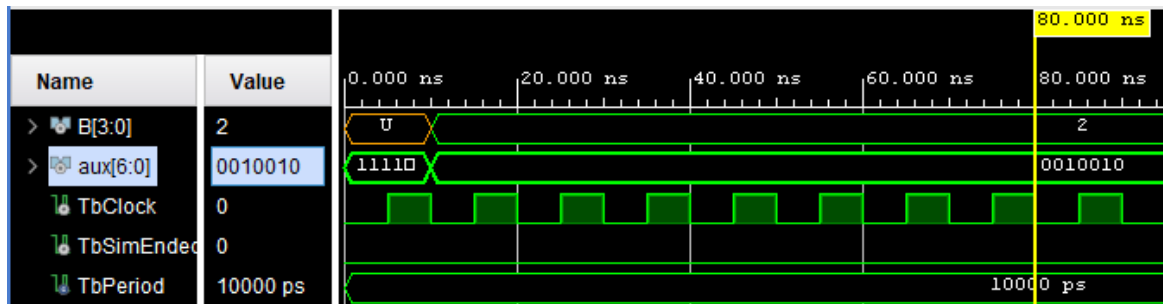


Diagrama RTL

 

## CartaASM

## Código de implementación

```

library IEEE;
library work;

use IEEE.STD_LOGIC_1164.ALL;
use work.mypackage.ALL;

```

```
entity cartaASM is
Port ( clr, clk : in  STD_LOGIC;
      ini : in  STD_LOGIC;
      dato : in  STD_LOGIC_VECTOR (8 downto 0);
      dato1 : out  STD_LOGIC_VECTOR (8 downto 0);
      display : out  STD_LOGIC_VECTOR (6 downto 0));
end cartaASM;
```

```
architecture Behavioral of cartaASM is
```

```
signal lb, eb, la, ea, ec, a0, z : STD_LOGIC;
signal B : STD_LOGIC_VECTOR (3 downto 0);
signal aux : STD_LOGIC_VECTOR (6 downto 0);
begin
```

```
    unic : ctrlUnit port map (
        clk => clk,
        clr => clr,
        ini => ini,
        a0 => a0,
        z => z,
        la => la,
        ea => ea,
        eb => eb,
        lb => lb,
        ec => ec
    );
```

```
    reg : arreglo port map (
        clk => clk,
        clr => clr,
        la => la,
        ea => ea,
        dato => dato,
        dato1 => dato1,
        z => z,
        a0 => a0
    );
```

```
    conta : Contador port map (
        clk => clk,
        clr => clr,
        lb => lb,
        eb => eb,
        B => B
    );
```



```

    deco : Decodificador port map (
        B => B,
        aux => aux
    );

    mux : multiplexor port map (
        aux => aux,
        ec => ec,
        display => display
    );

end Behavioral;

```

Código de simulación

```

library ieee;
use ieee.std_logic_1164.all;

entity tb_cartaASM is
end tb_cartaASM;

architecture tb of tb_cartaASM is

    component cartaASM
        port (clr      : in std_logic;
              clk      : in std_logic;
              ini      : in std_logic;
              dato      : in std_logic_vector (8 downto 0);
              dato1     : out std_logic_vector (8 downto 0);
              display   : out std_logic_vector (6 downto 0));
    end component;

    signal clr      : std_logic;
    signal clk      : std_logic;
    signal ini      : std_logic;
    signal dato      : std_logic_vector (8 downto 0);
    signal dato1     : std_logic_vector (8 downto 0);
    signal display   : std_logic_vector (6 downto 0);

    constant TbPeriod : time := 100 ns; -- EDIT Put right period here
    signal TbClock : std_logic := '0';
    signal TbSimEnded : std_logic := '0';

begin

    dut : cartaASM
        port map (clr      => clr,
                  clk      => clk,
                  ini      => ini,

```

```

        dato    => dato,
        dato1    => dato1,
        display => display);

-- Clock generation
TbClock <= not TbClock after TbPeriod/2 when TbSimEnded /= '1' else '
0';

-- EDIT: Check that clk is really your main clock signal
clk <= TbClock;

stimuli : process
begin

    ini <= '0';

    --dato <= "101101011";    --a
    --dato <= "000011101";    --b
    --dato <= "000010000";    --c
    --dato <= "100001000";    --d
    dato <= "000000000";    --e
    wait for 100ns;
    clr <= '0';
    ini <= '1';


    -- EDIT Add stimuli here
    wait for 12 * TbPeriod;

    -- Stop the clock and hence terminate the simulation
    TbSimEnded <= '1';
    wait;
end process;

end tb;


```

Diagrama RTL

 

3. Simular el funcionamiento de la arquitectura completa con los siguientes valores para el registro, todos los estímulos deberán ser cargados desde test-bench


a. 101101011

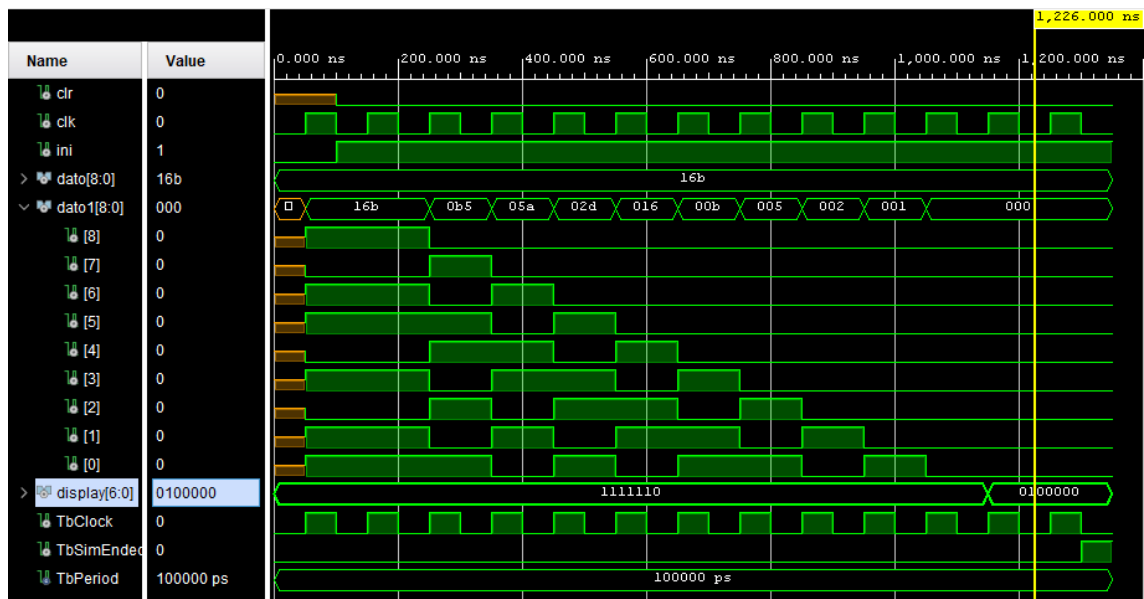

Observamos como la salida llamada dato 1 va cambiando hasta llegar a ser completamente 0, es decir que podemos observar como se realiza el desplazamiento.


Además, a la salida del display podemos observar el vector “0100000”, y dado que el display es uno de ánodo común, cada 0 indica el segmento encendido, teniendo en este caso a la salida el número 6.

b. 000011101

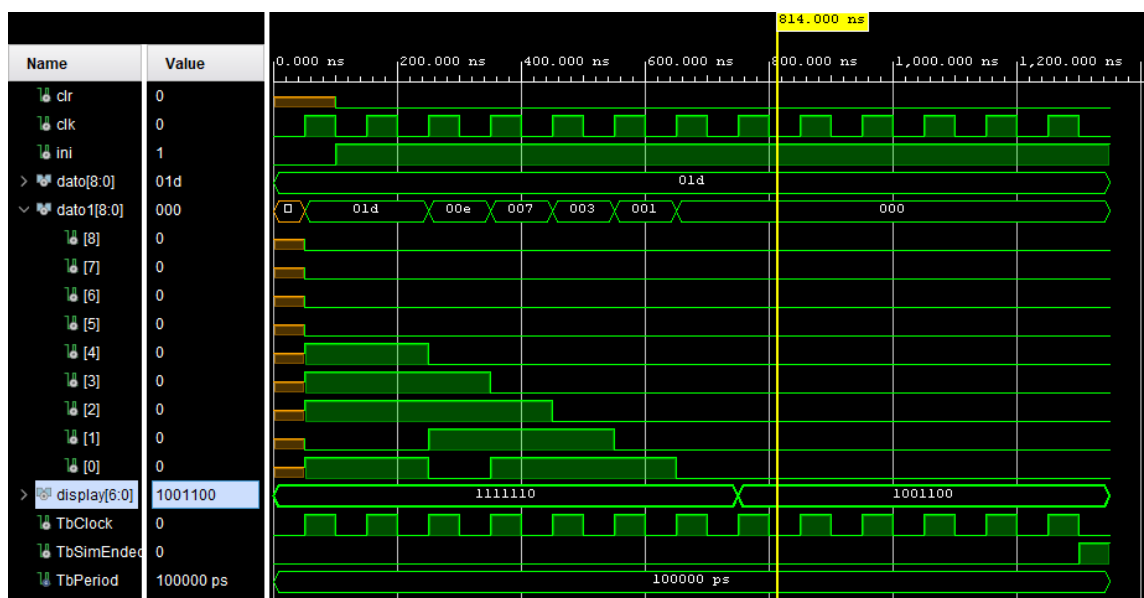


Observamos que la salida del display tiene el vector “1001100”. Dado que trabajamos con display de ánodo común, este sería el equivalente al número 4. El cual corresponde al número de unos existentes en el vector de entrada.

c. 000010000

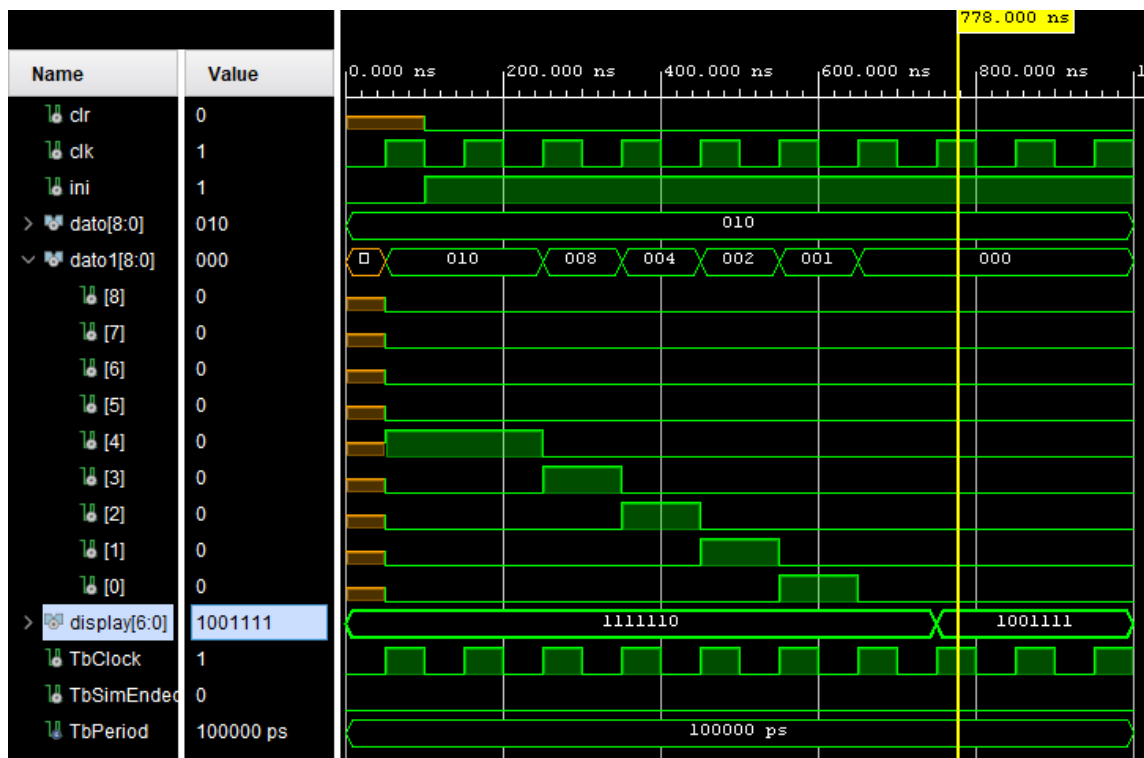


Observamos como el uno se va desplazando a lo largo de la ejecución del programa, además observamos que a la salida obtenemos el vector “1001111”, el cual corresponde a un 1 mostrado en un display de ánodo común.

d. 100001000

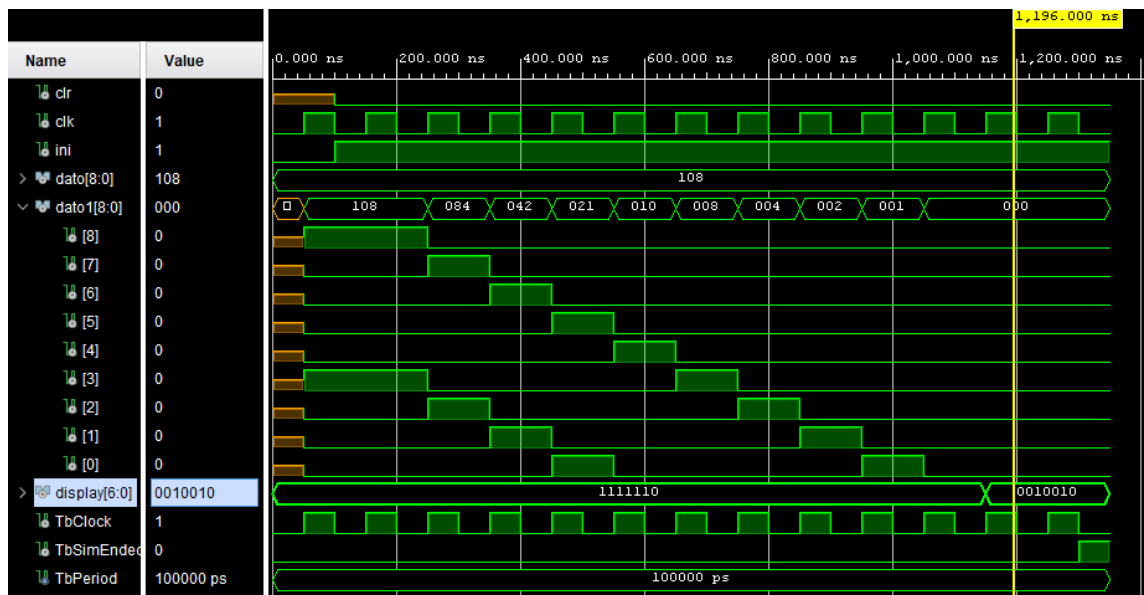

Observamos como se realiza el desplazamiento de bits, además a la salida notamos que tenemos el vector “0010010” el cual corresponde a la representación de un numero 2 mostrado en un display de ánodo común.

e. 000000000

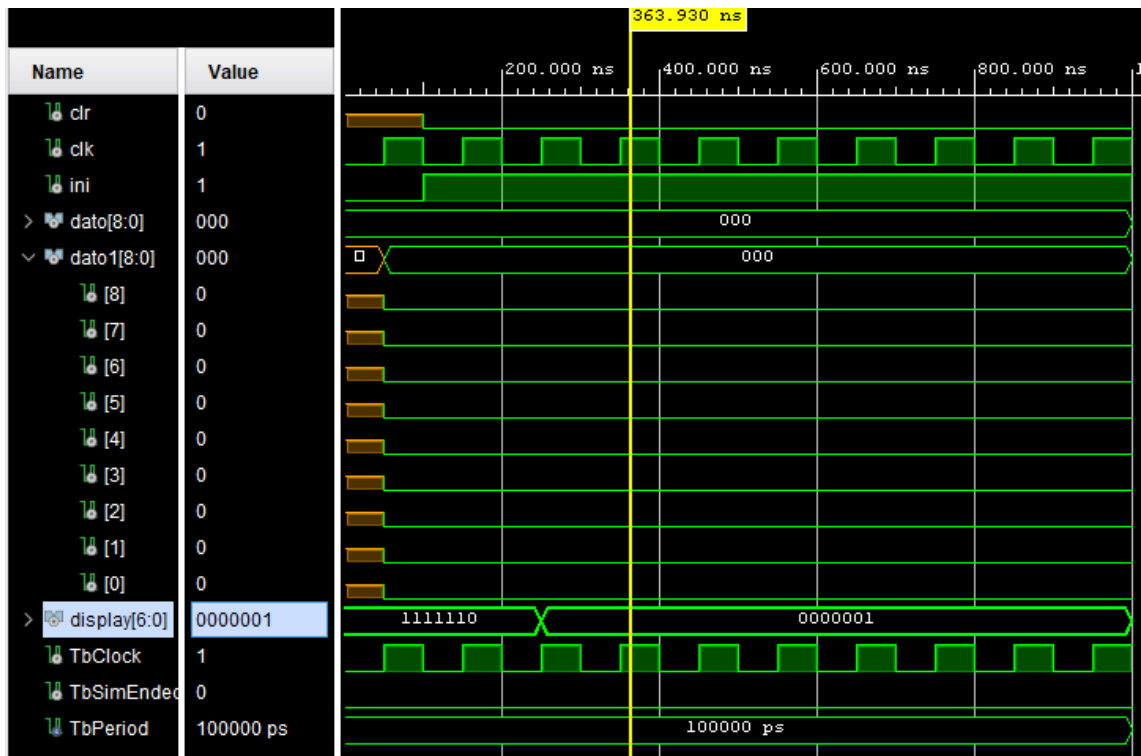

Observamos que se verifica inmediatamente que el dato de entrada es 0, por lo cual se obtiene pronto a la salida el vector “0000001”, el cual es la representación de un 0 en un display de ánodo común.